


Lab 1

Sami Elias, Joseph popoviciu

Objective

Create 3x8 decoder using

Generate function

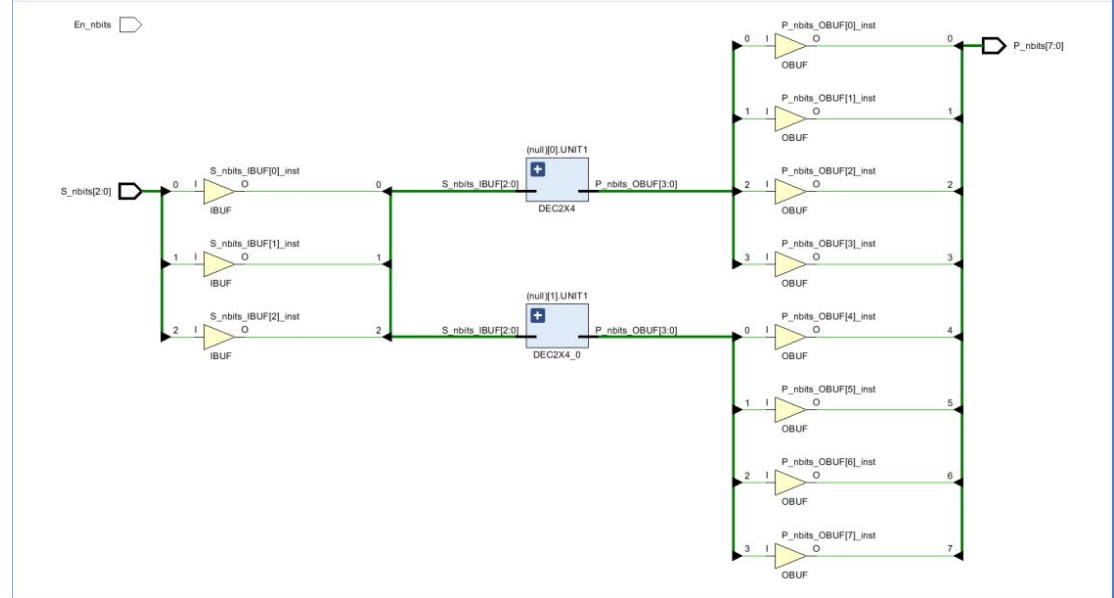

Generate function

This was the generate
Function we used to help
Build the decoder.


```
genvar i;  
generate  
if(DATA_WIDTH%2==1)//odd #ofinputs  
begin  
wire [1:0] temp_nbits;  
assign temp_nbits[0]=~S_nbits[DATA_WIDTH-1];  
assign temp_nbits[1]=S_nbits[DATA_WIDTH-1];  
for(i=0;i<(2**DATA_WIDTH)/4;i=i+1)  
begin  
    DEC2X4 UNIT1  
    (  
        .S(S_nbits[1:0]),  
        .P(P_nbits[4*i+3:4*i]),  
        .En(temp_nbits[i])
```

Problems


One problem we had was after we figured out the generate function, the code would not run properly and we did not know what was wrong. We found the solution was to add an if statement after.

```
genvar i;
generate
if(DATA_WIDTH%2==1)//odd #ofinputs
begin
wire [1:0] temp_nbits;
assign temp_nbits[0]=~S_nbits[DATA_WIDTH-1];
assign temp_nbits[1]=S_nbits[DATA_WIDTH-1];
    for(i=0;i<(2*(DATA_WIDTH)/4;i=i+1)
        begin
            DEC2X4 UNIT1
            (
                .S(S_nbits[1:0]),
                .P(P_nbits[4*i+3:4*i]),
                .En(temp_nbits[i])
            );
        end
    end
else if(DATA_WIDTH%2==0 && DATA_WIDTH==2)//even2x4
begin
    DEC2X4 UNIT0
    (
        .S(S_nbits[DATA_WIDTH-1:DATA_WIDTH-2]),
        .P(P_nbits),
        .En(En_nbits)
    );
end
endgenerate
```


Test bench

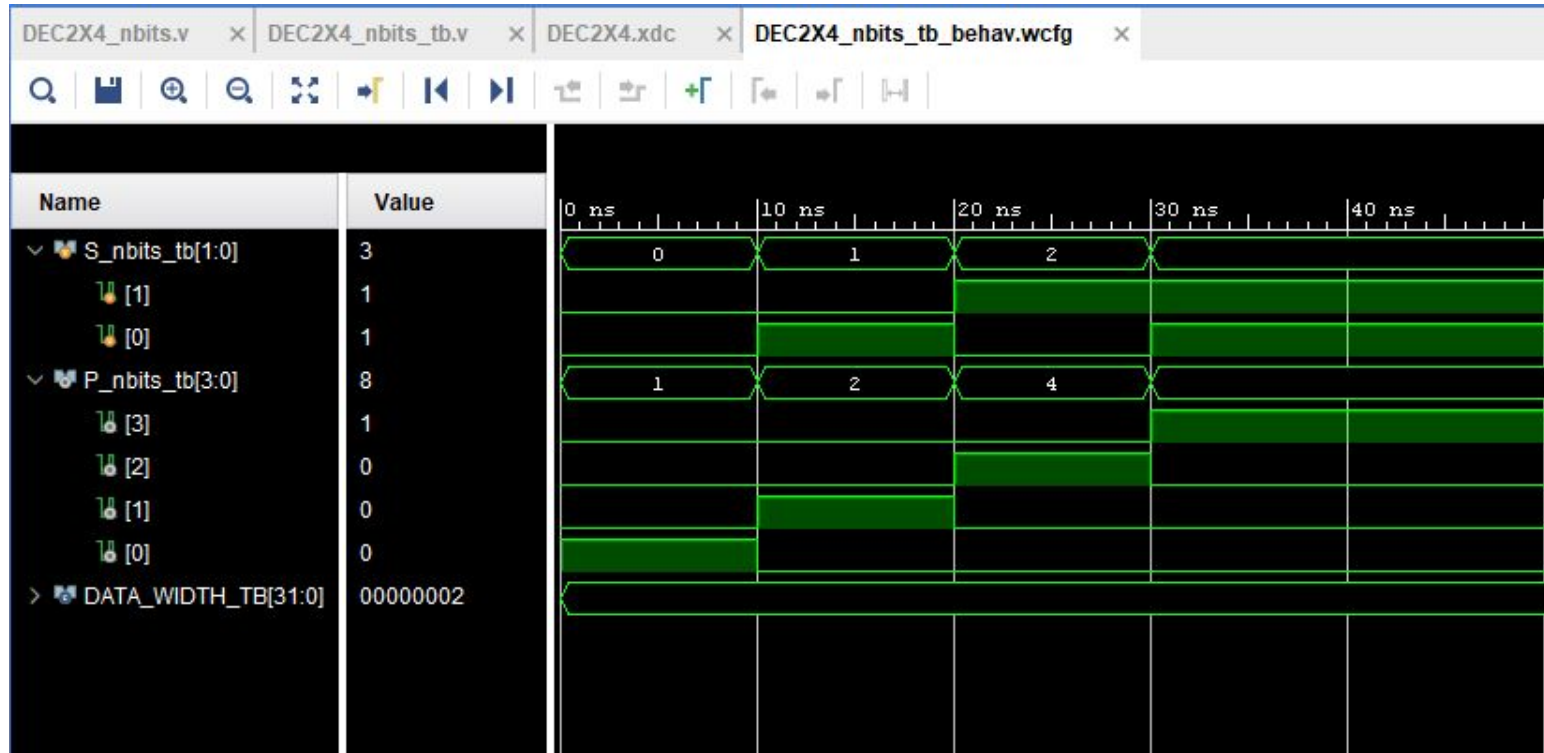

Test bench Cont.

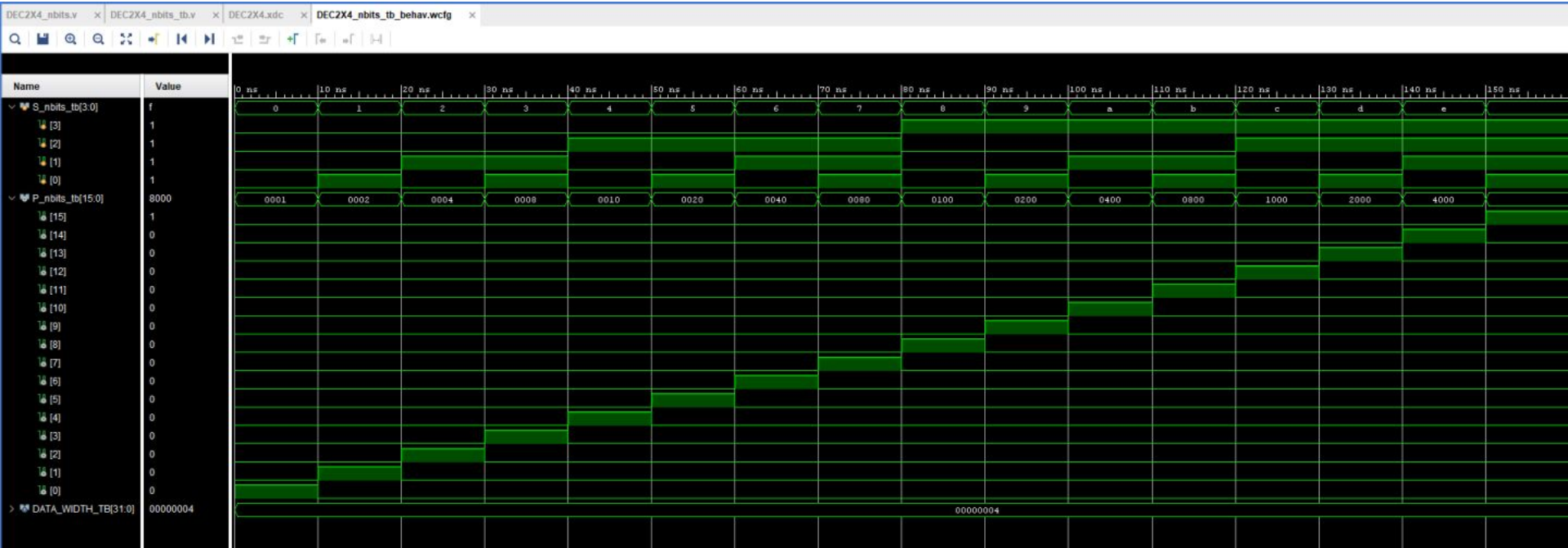

Results

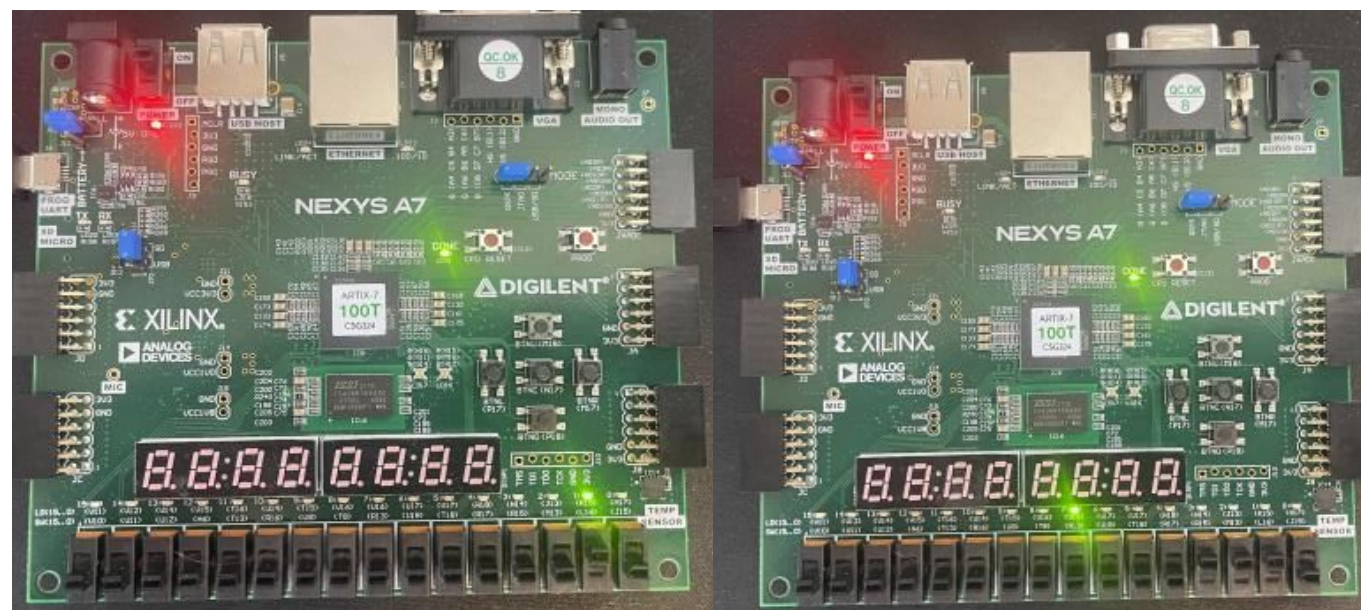

The image on the left shows the decoder at 01 and the image on the right shows it at 111 to show that it is fully functioning.