

ECE 3300L

Lab 2: Majority Encoder

Instructor: Dr. Mohamed Aly

Group A

Sami Elias	012546378	<a href="mailto:samielias@cpp.edu">samielias@cpp.edu</a>
------------	-----------	--

Joseph Popoviciu	014357772	<a href="mailto:jdpopoviciu@cpp.edu">jdpopoviciu@cpp.edu</a>
------------------	-----------	--

Objective:

The objective is to design a majority encoder using structural modeling with data flow.

Furthermore, we incorporate the majority encoder with our FA and FA\_nbits.

Procedure:

We first create a 3-bit majority encoder which calculates our carry out for a 1-bit full adder. Once we had the module for the majority encoder, we instantiated it within the 1-bit full adder which was already instantiated within the n-bit full adder.

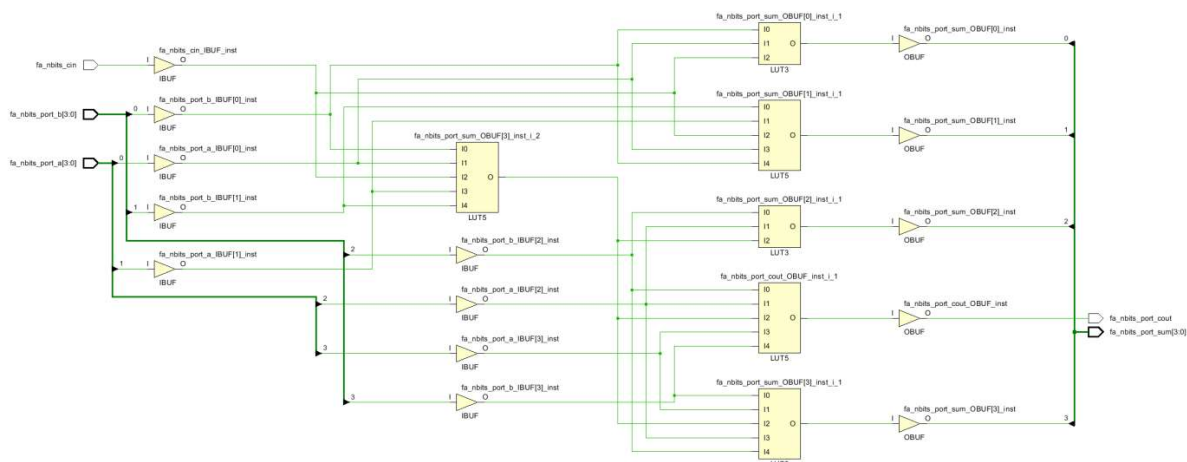


Figure 1- 4-bit Full Adder Schematic

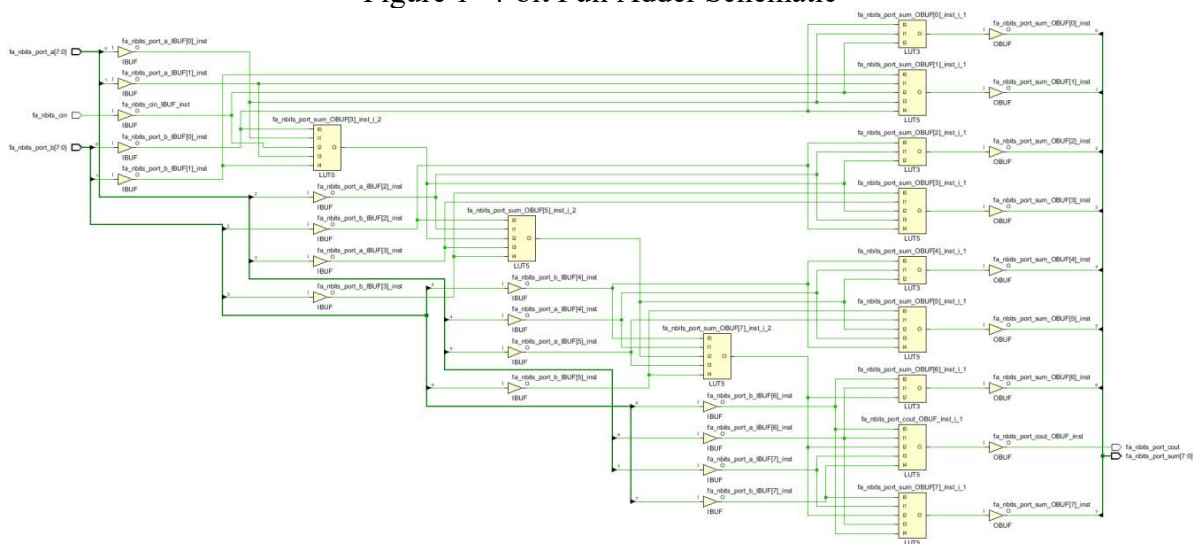


Figure 2- 8-bit Full Adder Schematic

After ensuring our code was correct with a testbench and simulation. Once the simulation was outputting the expected bits we began to synthesize, implement, and generate a bitstream.

As a result, we obtained schematics shown in figures 1 and 2 above.

Results:

 


Image 3 shows  $0100+0011$ , with the sum being  $0111$ .

 


Figure 4- FPGA Board Displaying 4-bit addition

Image 4 shows the same as image 3, but there is a carry in of 1 which results with the sum being  $1000$ .



 


Figure 5- FPGA Board Displaying 4-bit addition

In figure 5 we test the carry out. The LED on the far-left side of the FPGA board represents the carry out. To test our carry out we added 1011 with 0100 which resulted with a sum of 0001 and a carry out of 1.

Test bench:



Figure 6 - Vivado Behavioral Testbench

 


Figure 7 - Vivado Behavioral Testbench

 


Figure 8 - FPGA Utilization

## Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 8.733 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 64.8°C  
**Thermal Margin:** 20.2°C (4.4 W)  
**Effective  $\theta_{JA}$ :** 4.6°C/W  
**Power supplied to off-chip devices:** 0 W  
**Confidence level:** Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 


Figure 9 - FPGA Power Summary

## Contributions:

Joseph Popoviciu:

I primarily worked on the code, programmed the FPGA board, and created the video demo. I also helped with the lab report.

Sami Elias:

I assisted with the code, wrote the main points of the report, and did the majority of the PowerPoint.